

# PHYS 371 - Assignment III

Celil Buğra Karacan  
Department of Physics, Bilkent University  
(Dated: October 29, 2018)

## I. INTRODUCTION

### A. Question I

Calculating angles in FIG. 1. in terms of  $M_1, M_2, M_3; l_1, l_2, l_3, l_4$  was the assignment. System is in static equilibrium and ropes have their respective tensions:  $T_1, T_2, T_3, T_4$ .

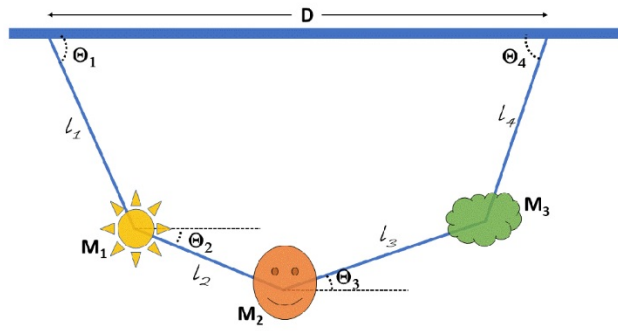


FIG. 1. Question-I diagram.

### B. Question II

Electrical circuit with six currents to be determined using given voltage and resistance values. Question explicitly suggested using matrices drawn from Kirchoff's laws.

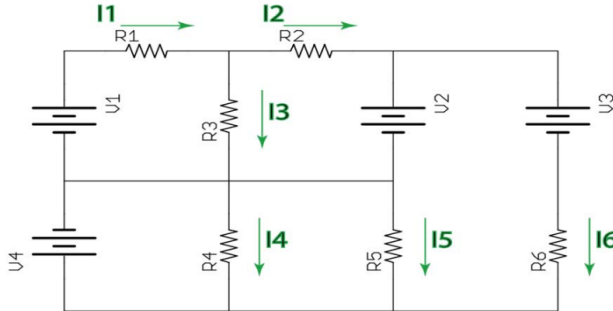


FIG. 2. Question-II diagram.

## II. METHOD

### A. Question I

Firstly free-body diagrams of all three objects were drawn and relations between  $M, l, T, \theta$  were questioned leading to following equalities:

$$\begin{bmatrix} M_1 g \\ M_2 g \\ M_3 g \end{bmatrix} = \begin{bmatrix} 1, -1, 0, 0 \\ 0, 1, 1, 0 \\ 0, 0, -1, 1 \end{bmatrix} \begin{bmatrix} T_1 \sin \theta_1 \\ T_2 \sin \theta_2 \\ T_3 \sin \theta_3 \\ T_4 \sin \theta_4 \end{bmatrix}$$

$$T_1 \cos \theta_1 = T_2 \cos \theta_2 = T_3 \cos \theta_3 = T_4 \cos \theta_4 \quad (*)$$

$$[l_1, l_2, l_3, l_4] * \begin{bmatrix} \cos \theta_1 \\ \cos \theta_2 \\ \cos \theta_3 \\ \cos \theta_4 \end{bmatrix} = D.$$

Multiplying D from left with pseudo-inverse of  $[l_1, l_2, l_3, l_4]$  shall give an approximation for  $\cos \theta_i$ . From there on  $\arccos()$  function can be utilized to find  $\theta_i$  values.

### B. Question II

After given constants were input, a matrix was formed as suggested.

$$\begin{bmatrix} R_1 & R_2 & 0 & 0 & 0 & R_6 \\ 0 & 0 & 0 & R_4 & -R_5 & 0 \\ 0 & 0 & 0 & 0 & -R_5 & R_6 \\ 0 & 0 & 0 & R_4 & 0 & 0 \\ R_1 & 0 & R_3 & 0 & 0 & 0 \\ 1 & -1 & -1 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \\ I_6 \end{bmatrix} = \begin{bmatrix} V_1 - V_3 - V_4 \\ 0 \\ V_2 - V_3 \\ -V_4 \\ V_1 \\ 0 \end{bmatrix}$$

Using `inv()` function of MATLAB® and matrix multiplication `Current` array was solved in amperes. Next part of the question asked for plotting current as a function of  $R_6$ . Which have been accomplished by defining  $R_6$  as symbolic variable and plotting  $P = I_6^2 * R_6$  using `ezplot()`.

### III. VERIFICATION OF THE PROGRAM

#### A. Question I

After calculating  $\theta_i$  values as dscribed, to check error equation (\*) will be used. As revealed after running the code, method used ended up with non-acceptable error:

$$T_i \cos \theta_i = T_i \sin \theta_i * \cot \theta_i$$

$$T_1 \cos \theta_1 = 34.0699$$

$$T_1 \cos \theta_2 = 6.0866$$

$$T_1 \cos \theta_3 = 7.2170$$

$$T_1 \cos \theta_4 = 86.5348$$

(for  $l_1 = 3, l_2 = 2, l_3 = 4, l_4 = 5, M_1 = 5, M_2 = 3, M_3 = 7, D = 8$ )

#### B. Question II

Taking special case of  $V_4 = 0V$  into consideration, one expects  $I_4 = I_5 = 0\Omega$ . Since for resistances mentioned would have same potential at both of their respective ends. Program returns these values for currents:

$$I_1 = -0.0909, I_2 = -0.4545, I_3 = 0.3636,$$

$$I_4 = 0, I_5 = 0, I_6 = -0.1667$$

### IV. DATA

#### A. Question I

There were no plots drawn, and data was not prone to error, thus not included.

#### B. Question II

For the first part following data was acquired:

$$I_1 = -0.0909, I_2 = -0.4545, I_3 = 0.3636,$$

$$I_4 = -1.0000, I_5 = -0.8000, I_6 = -0.8333$$

For the second part the figure (FIG.3.) is placed below.

### V. ANALYSIS

#### A. QuestionII

As seen in FIG. 3. as  $R_6$  decreases towards zero, dissipation power peaks enourmously. This is analuguous to a short-cut in circuit.

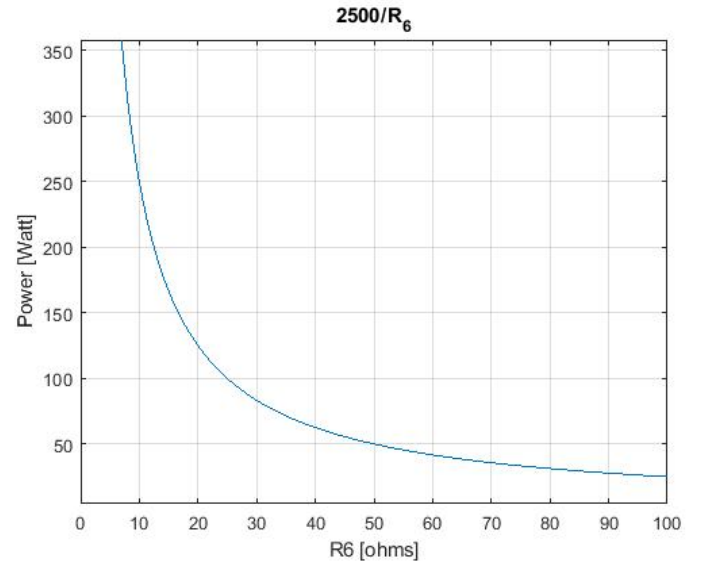


FIG. 3. Question-II plot

### VI. INTERPRETATION